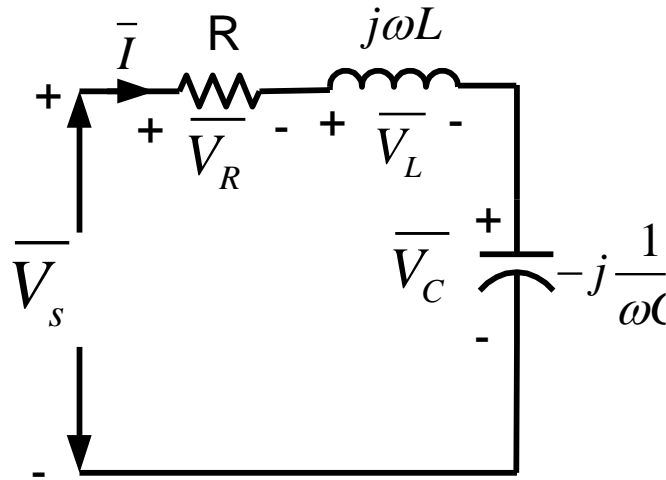


Introduction to Electrical Engineering

EE 103

Lecture 15

Phasor representation of circuits having sinusoidal forcing function under steady state operation




Applying KVL



$$\bar{V}_s = \bar{V}_R + \bar{V}_L + \bar{V}_C$$

$$\bar{V}_s = R\bar{I} + jX_L\bar{I} - jX_C\bar{I}$$

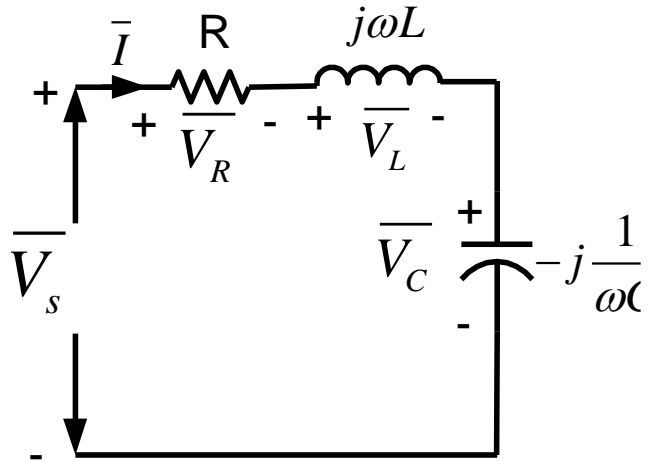
Technique for Phasor analysis of series circuits



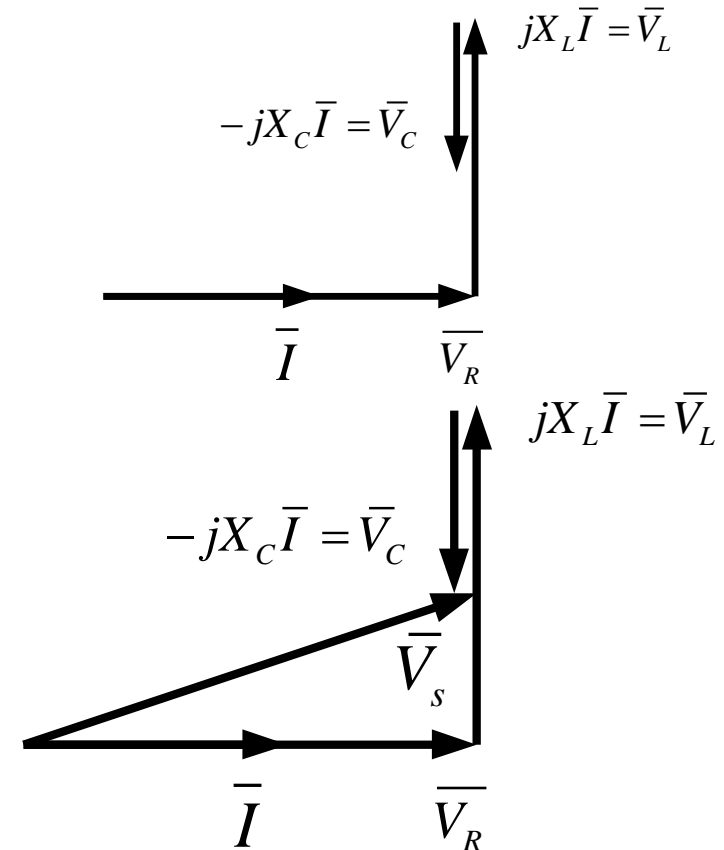
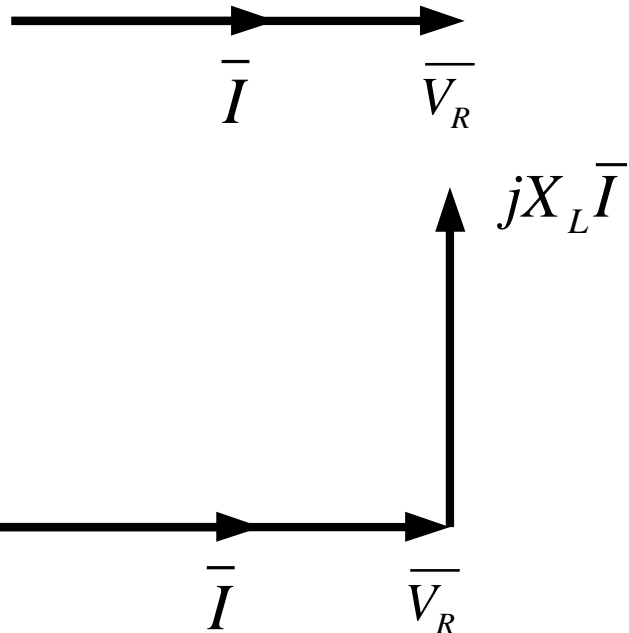
If \bar{I} is chosen as a reference phasor, analysis becomes easier



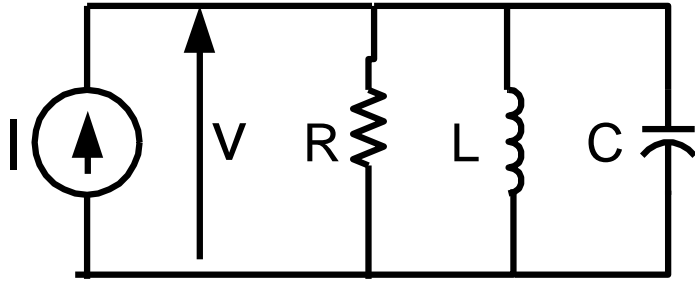Technique for Phasor analysis of parallel circuits



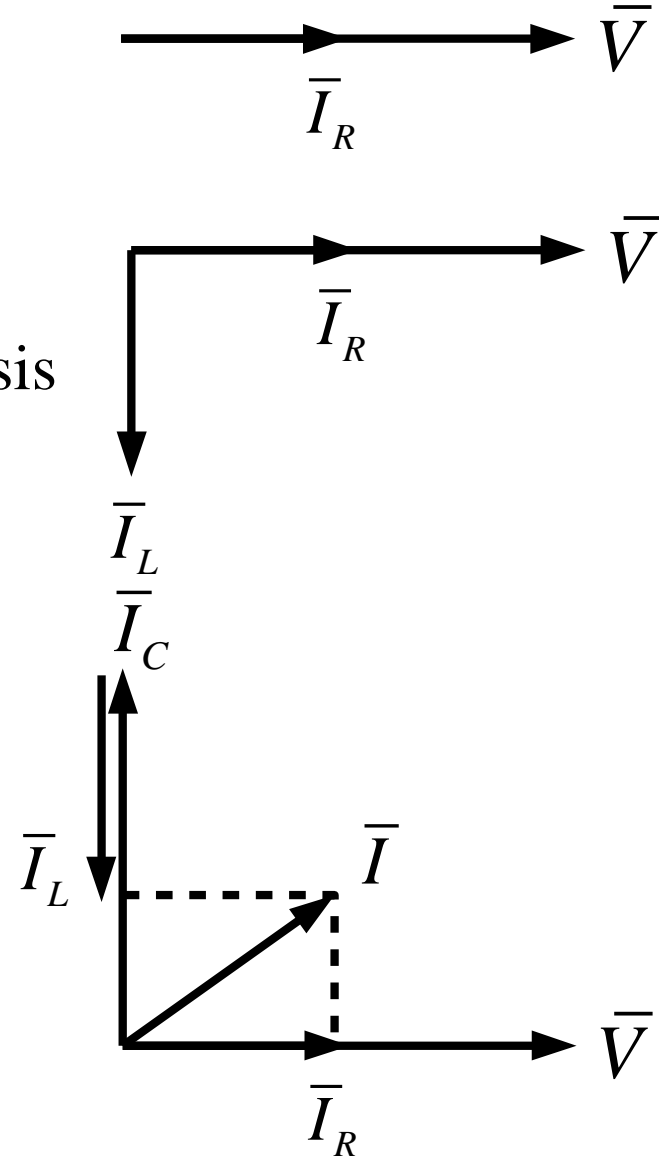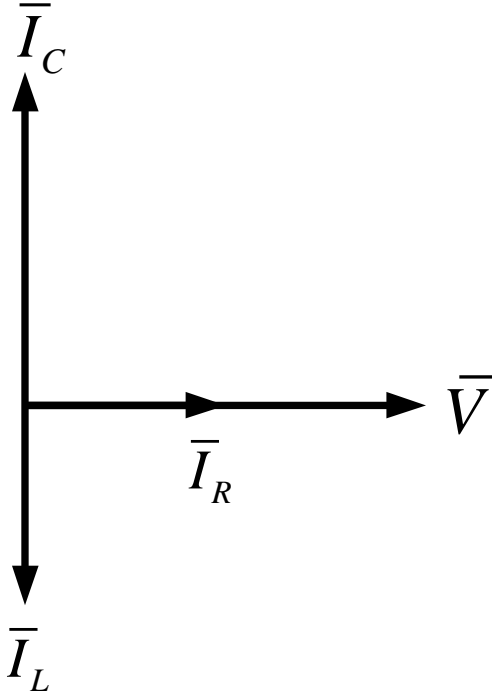If \bar{V} is chosen as a reference phasor, analysis becomes easier



Maximum Power Transfer Theorem


$$\bar{I} = \frac{\bar{V}}{(R_s + R_L) + j(X_s + X_L)}$$

$$|\bar{I}|^2 = \frac{V^2}{(R_s + R_L)^2 + (X_s + X_L)^2}$$

Power dissipated in the load,

$$P = \frac{V^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2}$$

$$P = f(R_L, X_L)$$

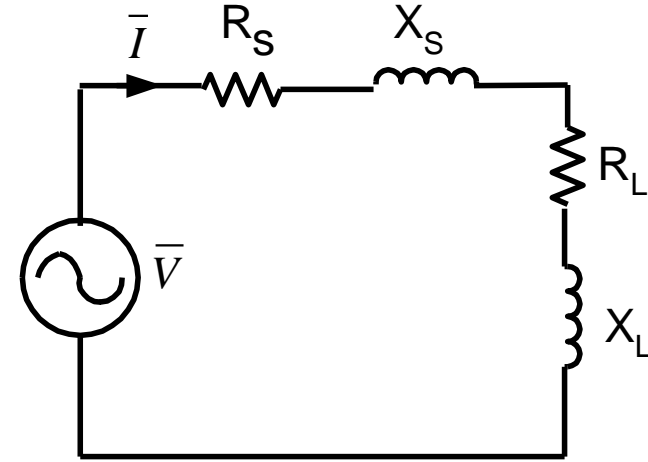

$$P = \frac{V^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2} \quad P = f(R_L, X_L)$$

$$\frac{\partial P}{\partial R_L} = 0 \quad \Rightarrow \quad \frac{V^2 \left[(R_s + R_L)^2 + (X_s + X_L)^2 - 2R_L (R_s + R_L) \right]}{\left[(R_s + R_L)^2 + (X_s + X_L)^2 \right]^2} = 0 \quad (1)$$

$$\frac{\partial P}{\partial X_L} = 0 \quad \Rightarrow \quad \frac{V^2 R_L \left[-2R_L (X_s + X_L) \right]}{\left[(R_s + R_L)^2 + (X_s + X_L)^2 \right]^2} = 0 \quad (2)$$

$$\text{From (2)} \quad X_L = -X_s \quad (3)$$

Putting (3) in (1)


$$R_L = R_s$$

$$X_L = -X_s$$

$$R_L = R_s$$

Or

$$\overline{Z}_L = \overline{Z}_s^*$$

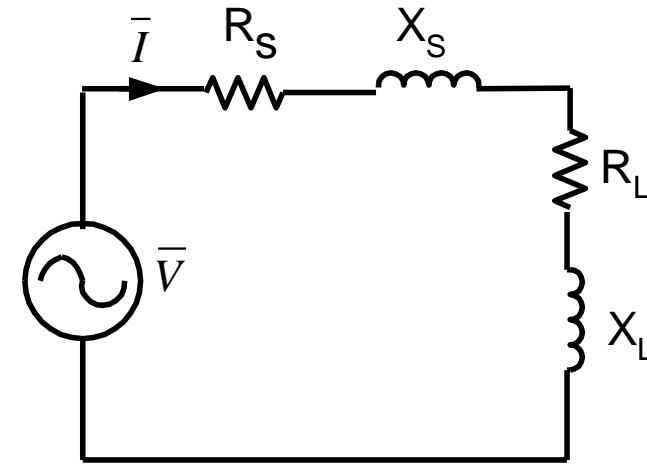

If only R_L is allowed to vary
then from (1), keeping
 X_L and X_s fixed,

$$R_L = \sqrt{R_s^2 + (X_s + X_L)^2}$$

Resonance: Steady state operation of a system (circuit) at that frequency for which the resultant response is in time phase with the source function.


Series Resonance

$$I = \frac{\bar{V}_s}{R + j\left(\omega_0 L - \frac{1}{\omega_0 C}\right)}$$

$$\omega_0 L - \frac{1}{\omega_0 C} = 0$$

$$\omega_0^2 = \frac{1}{LC}$$





$$\omega_0 = \sqrt{\frac{1}{LC}}$$

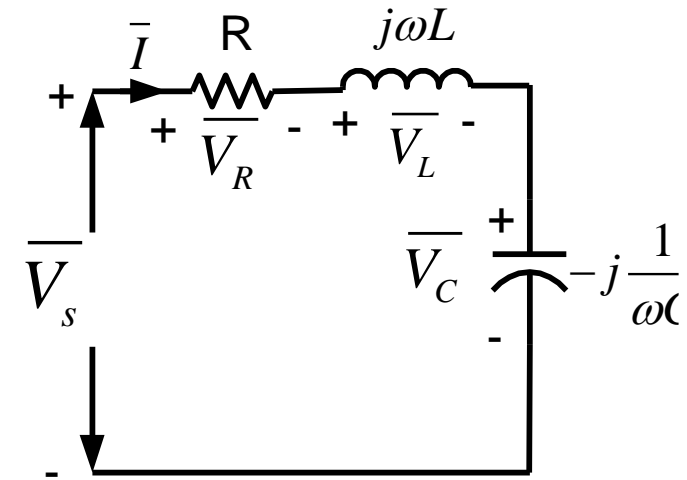

$$f_0 = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$$

ω_0 , resonant frequency decided by circuit parameters

Series Resonance

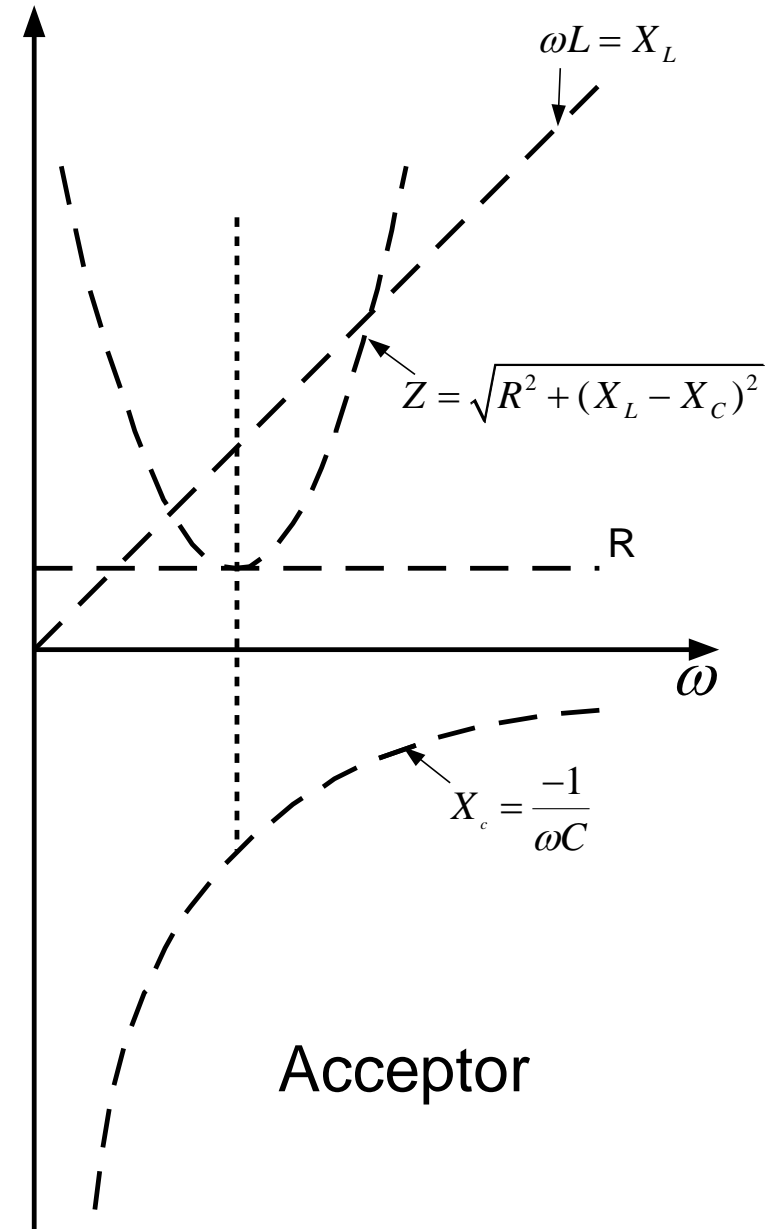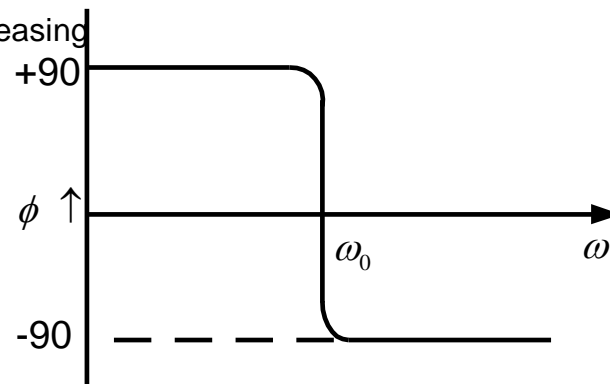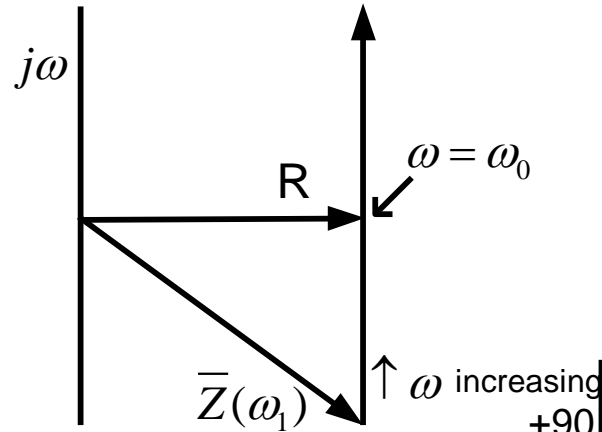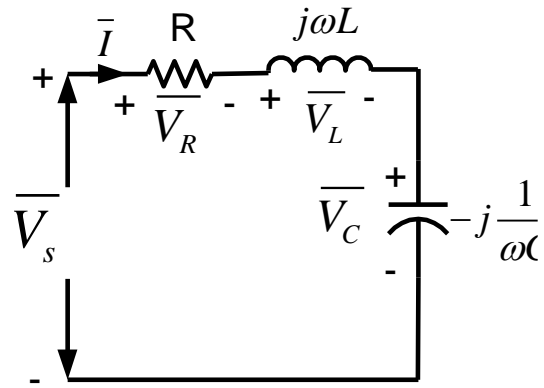

Parallel Resonance


$$\bar{Y} = G + jB$$

$$= \frac{1}{R} + j\left(-\frac{1}{\omega L} + \omega C\right)$$



\bar{I} and \bar{V} will be in phase when

$$\omega L = \frac{1}{\omega C} \qquad \omega = \frac{1}{\sqrt{LC}}$$

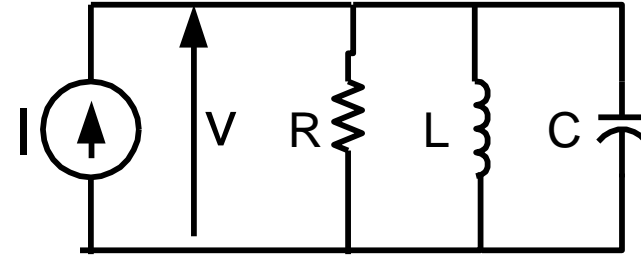
$$\bar{I} = \bar{V} \left\{ \frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right) \right\}$$



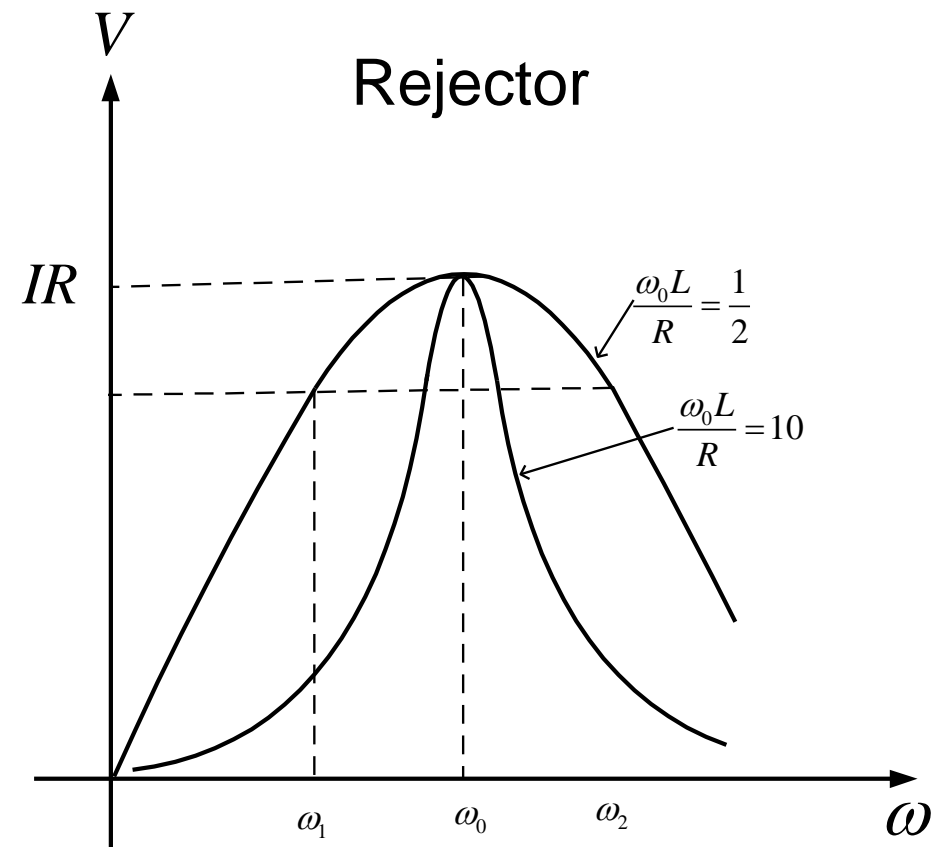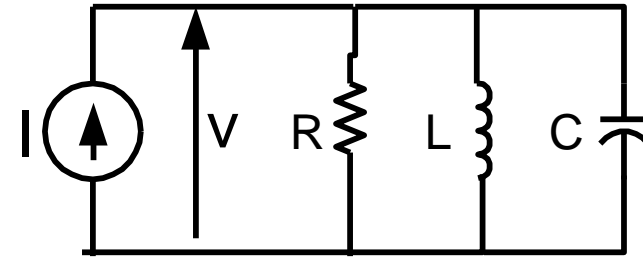Power delivered at resonance $P_0 = V_0 I_0$
 $= \frac{V_0^2}{R}$




Star-Delta Transformation

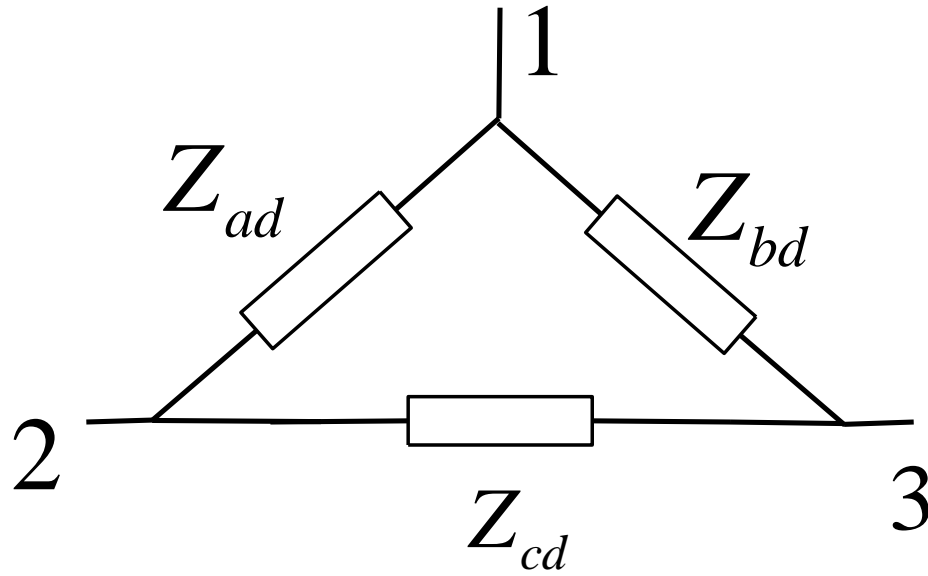

$$\bar{Z}_{as} = \frac{\bar{Z}_{ad} \bar{Z}_{bd}}{\bar{Z}_{ad} + \bar{Z}_{bd} + \bar{Z}_{cd}}$$

$$\bar{Z}_{bs} = \frac{\bar{Z}_{ad} \bar{Z}_{cd}}{\bar{Z}_{ad} + \bar{Z}_{bd} + \bar{Z}_{cd}}$$
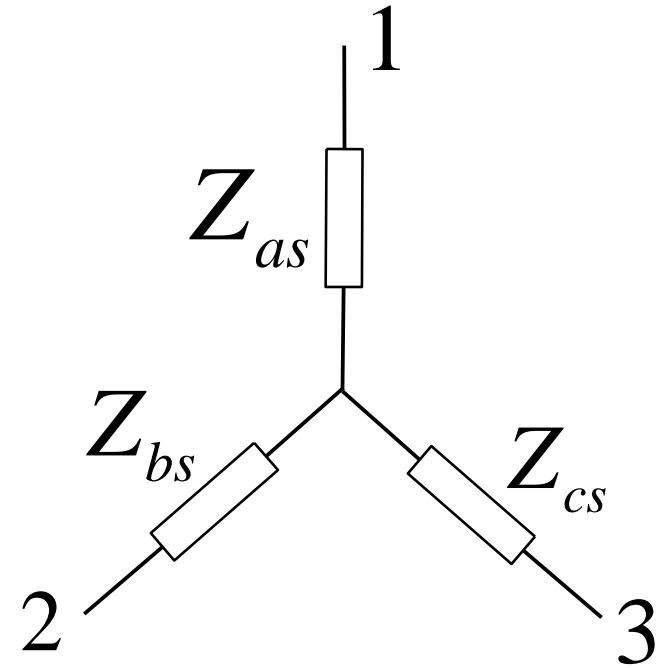
$$\bar{Z}_{cs} = \frac{\bar{Z}_{cd} \bar{Z}_{bd}}{\bar{Z}_{ad} + \bar{Z}_{bd} + \bar{Z}_{cd}}$$



$$\bar{Z}_{ad} = \frac{\bar{Z}_{as} \bar{Z}_{bs} + \bar{Z}_{bs} \bar{Z}_{cs} + \bar{Z}_{cs} \bar{Z}_{as}}{\bar{Z}_{cs}}$$

$$\bar{Z}_{bd} = \frac{\bar{Z}_{as} \bar{Z}_{bs} + \bar{Z}_{bs} \bar{Z}_{cs} + \bar{Z}_{cs} \bar{Z}_{as}}{\bar{Z}_{bs}}$$

$$\bar{Z}_{cd} = \frac{\bar{Z}_{as} \bar{Z}_{bs} + \bar{Z}_{bs} \bar{Z}_{cs} + \bar{Z}_{cs} \bar{Z}_{as}}{\bar{Z}_{as}}$$

Control of Systems: Control Engineering

Laplace Transformation

Pierre-Simon Laplace

Article Talk

Read Edit View history Tools ▼

From Wikipedia, the free encyclopedia

"Laplace" redirects here. For other uses, see [Laplace \(disambiguation\)](#).

Pierre-Simon, Marquis de Laplace (/ləˈplɑːs/; French: [pjɛʁ simɔ̃ laplas]; 23 March 1749 – 5 March 1827) was a French [polymath](#), a [scholar](#) whose work has been instrumental in the fields of [physics](#), [astronomy](#), [mathematics](#), [engineering](#), [statistics](#), and [philosophy](#). He summarized and extended the work of his predecessors in his five-volume *Mécanique céleste* (*Celestial Mechanics*) (1799–1825). This work translated the geometric study of [classical mechanics](#) to one based on [calculus](#), opening up a broader range of problems. Laplace also popularized and further confirmed [Sir Isaac Newton's](#) work.^[2] In statistics, the [Bayesian interpretation](#) of probability was developed mainly by Laplace.^[3]

Laplace formulated [Laplace's equation](#), and pioneered the [Laplace transform](#) which appears in many branches of [mathematical physics](#), a field that he took a leading role in forming. The [Laplacian differential operator](#), widely used in mathematics, is also named after him. He restated and developed the [nebular hypothesis](#) of the [origin of the Solar System](#) and was one of the first scientists to suggest an idea similar to that of a [black hole](#),^[4] with [Stephen Hawking](#) stating that "Laplace essentially predicted the existence of black holes".^[1] He originated [Laplace's demon](#), which is a hypothetical all-predicting intellect. He also refined Newton's calculation of the [speed of sound](#) to derive a more

Pierre-Simon Laplace



Pierre-Simon Laplace as chancellor of the Senate under the [First French Empire](#)

Born	23 March 1749 <div>Beaumont-en-Auge, Normandy, Kingdom of France</div>
Died	5 March 1827 (aged 77)

$$\mathcal{L}[f(t)] = F(s) = \int_{0^-}^{\infty} f(t) e^{-st} dt$$

$$s = \sigma + j\omega$$

Inverse Laplace transform

$$\mathcal{L}^{-1}\{\mathcal{L}[f(t)]\} = \mathcal{L}^{-1}[F(s)] = f(t)$$

Inverse Laplace transform


$$f(t) = \frac{1}{2\pi j} \int_{c-j\infty}^{c+j\infty} F(s) e^{st} ds$$

1) Transform pair

$$f(t) = 1$$

$$\therefore \mathcal{L}[1] = \int_0^{\infty} e^{-st} dt = \left[-\frac{1}{s} e^{-st} \right]_0^{\infty} = \frac{1}{s}$$

For a unit step function

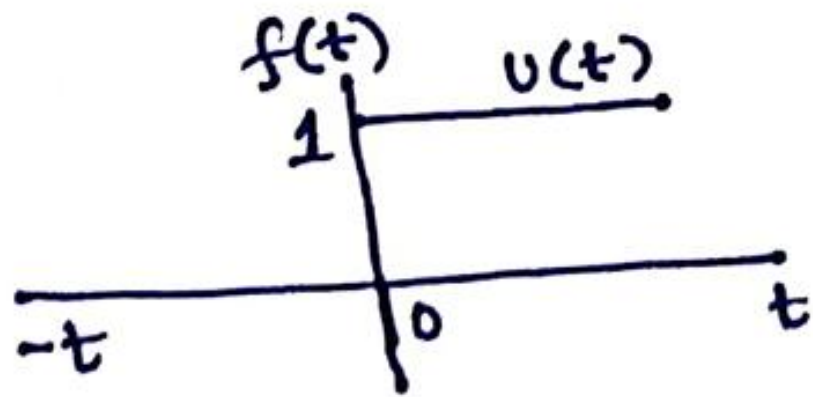

$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$$

$$\mathcal{L}[Vu(t)] = \frac{V}{s} \quad \leftarrow \frac{\text{transform}}{\text{pair}}$$

2) Another Transform Pair

$$f(t) = e^{at}$$

$$\mathcal{L}[e^{at}] = \int_{0^-}^{\infty} e^{at} \cdot e^{-st} dt = \int_{0^-}^{\infty} e^{-(s-a)t} dt$$

$$= \frac{1}{s-a}$$

$$e^{at} \longleftrightarrow \frac{1}{s-a}$$

transform pair

3) $f(t) = \sin \omega t$ \leftarrow Another Transform Pair

$$\mathcal{L}[\sin \omega t] = \int_{0^-}^{\infty} \sin \omega t e^{-st} dt$$

$$= \left[\frac{e^{-st} (-s \sin \omega t - \omega \cos \omega t)}{s^2 + \omega^2} \right]_{0^-}^{\infty}$$

$$= \frac{\omega}{s^2 + \omega^2}$$

Table of Transform Pairs

$f(t)$	$F(s)$
$u(t)$	$\frac{1}{s}$
e^{at}	$\frac{1}{s-a}$
$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$

Basic theorems :

(1) Transforms of linear combinations
$$\mathcal{L}[a_1 f_1(t) + a_2 f_2(t)] = a_1 F_1(s) + a_2 F_2(s)$$

Applicability of KCL and KVL

Basic theorems :

(2) Transform of Derivatives

$$[i] \quad \mathcal{L} \left[\frac{d}{dt} f(t) \right] = \int_{0^-}^{\infty} \frac{d}{dt} f(t) e^{-st} dt$$

$$\text{Let } u = e^{-st} \quad du = df(t)$$

$$du = -s e^{-st} dt \quad u = f(t)$$

$$\therefore \mathcal{L} \left[\frac{d}{dt} f(t) \right] = \left[e^{-st} f(t) \right]_{0^-}^{\infty} + s \int_{0^-}^{\infty} f(t) e^{-st} dt$$

$$= s F(s) - f(0^-)$$

[ii] Transform of the second derivative

$$\frac{d^2}{dt^2} f(t) = \frac{d}{dt} \frac{d}{dt} f(t)$$

$$\mathcal{L} \left[\frac{d^2 f(t)}{dt^2} \right] = s \mathcal{L} \left[\frac{d}{dt} f(t) \right] - \frac{d}{dt} f(0^-)$$

$$= s \left[s F(s) - f(0^-) \right] - \frac{d}{dt} f(0^-)$$

$$= s^2 F(s) - s f(0^-) - \frac{d}{dt} f(0^-)$$

$\frac{d}{dt} f(0^-) \Rightarrow$ derivative of $f(t)$
evaluated at $t=0$

The general expression for an n^{th} order derivative

$$\mathcal{L}\left[\frac{d^n f(t)}{dt^n}\right] = s^n F(s) - s^{n-1} f(0^-) - s^{n-2} \frac{d}{dt} f(0^-) - \dots - \frac{d^{n-1}}{dt^{n-1}} f(0^-)$$

(3) Transforms of integrals

$$\int_0^{\infty} f(t) e^{-st} dt = F(s)$$

integrating by parts \Rightarrow

$$F(s) = \underbrace{\left[e^{-st} \int f(t) dt \right]_{0^-}^{\infty}}_A + s \underbrace{\int_{0^-}^{\infty} \left[\int f(t) dt \right] e^{-st} dt}_B$$

$A = 0$ at $L = \infty$

The term B \Rightarrow

\therefore Rearranging

$$F(s) = -f^{(-1)}(0^-) +$$

$$\therefore \mathcal{L} \int f(t) dt = \frac{F(s)}{s} + \frac{f^{(-1)}(0^-)}{s}$$

Similarly

$$\mathcal{L} \iint f(t) dt = \frac{F(s)}{s^2} + \frac{f^{(-1)}(0^-)}{s^2} + \frac{f^{(-2)}(0^-)}{s}$$

at $t = 0^-$

$$A = \left. \int f(t) dt \right|_{t=0^-} = -f^{(-1)}(0^-)$$

= Value of the integral evaluated at $t = 0^-$ $= \int_{-\infty}^{0^-} f(t) dt$

$f^{(-1)}$ indicates integration


$$s \mathcal{L} \int f(t) dt$$

$$s \mathcal{L} \int f(t) dt$$

Similarly


$$\mathcal{L} \iint f(t) dt = \frac{F(s)}{s^2} + \frac{f^{(-1)}(0^-)}{s^2} + \frac{f^{(-2)}(0^-)}{s}$$

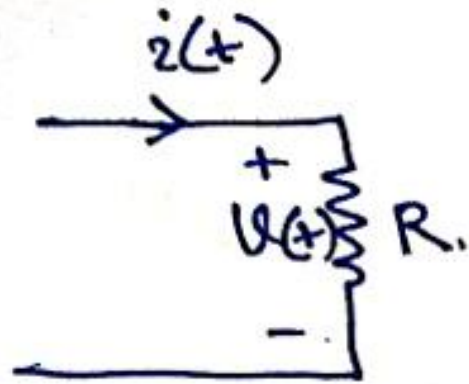Basic Circuit Elements in the Laplace Domain




$$v(t) = R i(t)$$
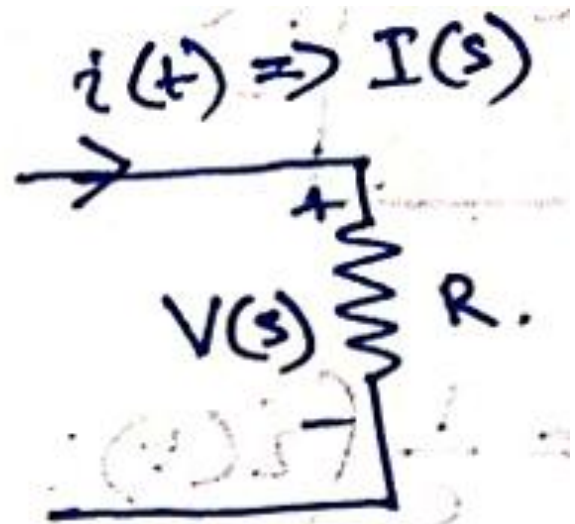
$$\mathcal{L}\{v(t)\} = \mathcal{L}\{R i(t)\}$$
$$V(s) = R I(s)$$



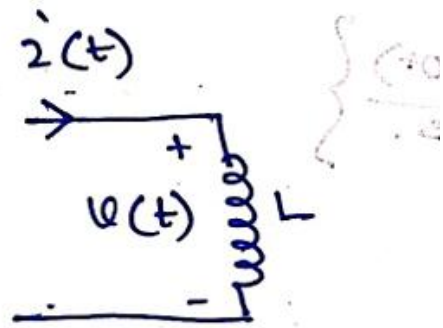Basic Circuit Elements in the Laplace Domain




$$v(t) = L \frac{di(t)}{dt}$$


$$\mathcal{L}\{v(t)\} = L \mathcal{L}\left\{\frac{di(t)}{dt}\right\}$$

$$V(s) = L\{s I(s) - I(0^-)\}$$


$$V(s) = sLI(s) - LI(0^-)$$

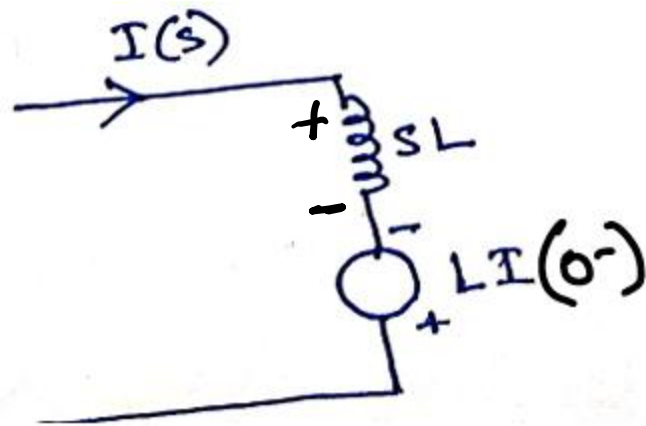

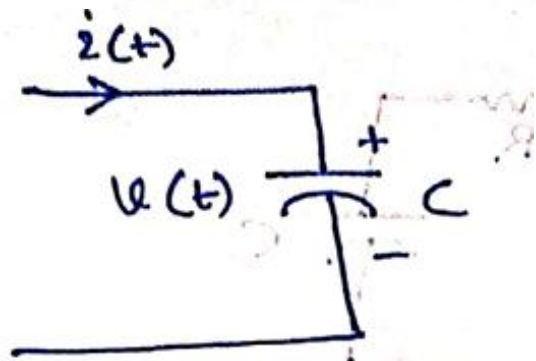Basic Circuit Elements in the Laplace Domain


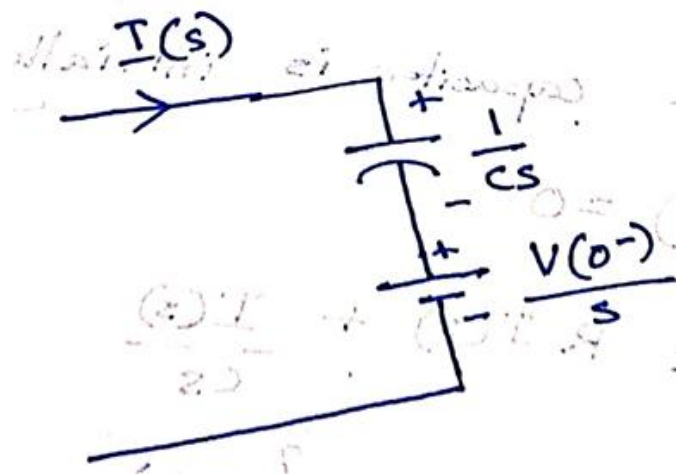
$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$



$$\mathcal{L}\{v(t)\} = \mathcal{L}\left[\frac{1}{C} \int_{-\infty}^t i(\tau) d\tau\right]$$

$$= \frac{1}{Cs} I(s) + \frac{1}{Cs} \int_{-\infty}^0 i(\tau) d\tau$$

$$v(0^-) = \frac{1}{C} \int_{-\infty}^0 i(\tau) d\tau$$

for Laplace transform

$$V(s) = \frac{1}{Cs} I(s) + \frac{1}{s} V(0^-)$$